

COVID-19 Return to Campus

Slide for use in Semester 2 classes



Protect yourself and others from getting sick



Stay home if you
feel unwell



Wash your hands
with soap



Cough into
your elbow



Avoid
contact



Use and dispose
of tissues



Stay 1.5m from
other people
where possible



Wipe down
any equipment
before use



Avoid crowding
around entryways before
and after classes



Follow lift etiquette
and use stairs
where possible

qut.edu.au/coronavirus

- Go to ***Return to campus resources and posters*** at [COVID-19: Information for staff](#)
- Contact your HSE Partners Amanda Burns or Matt Mackay for local area support and advice



School of Electrical Engineering and Robotics

EGB348 Electronics

Operational Amplifiers

Jasmine Banks (2020)

Recommended Readings:


Hambley: Chapter 14, Horowitz and Hill: Chapter 4

Operational Amplifiers


- An *operational amplifier* or *op amp* consists of ~20–30 transistors (BJTs or FETs), and a few resistors and capacitors, on a single IC.
- Op-amps have a wide range of general purpose applications.
- The term “Operational Amplifier” comes from the original application of the device in circuits to perform mathematical operations such as addition, subtraction, differentiation and integration.

Operational Amplifiers

- Terminals:

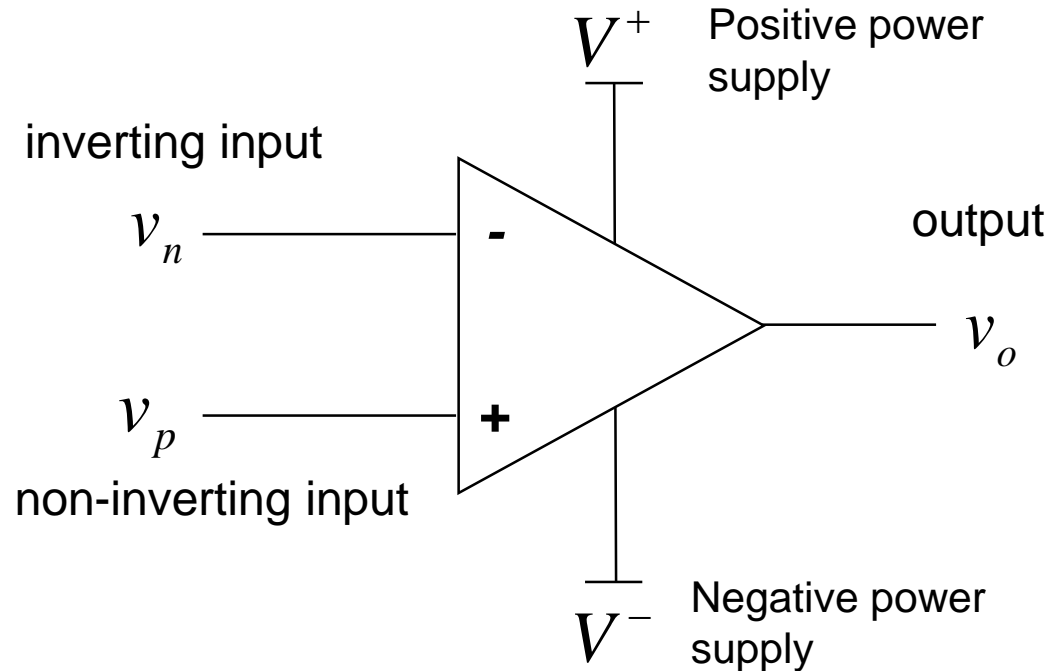

Operational Amplifiers

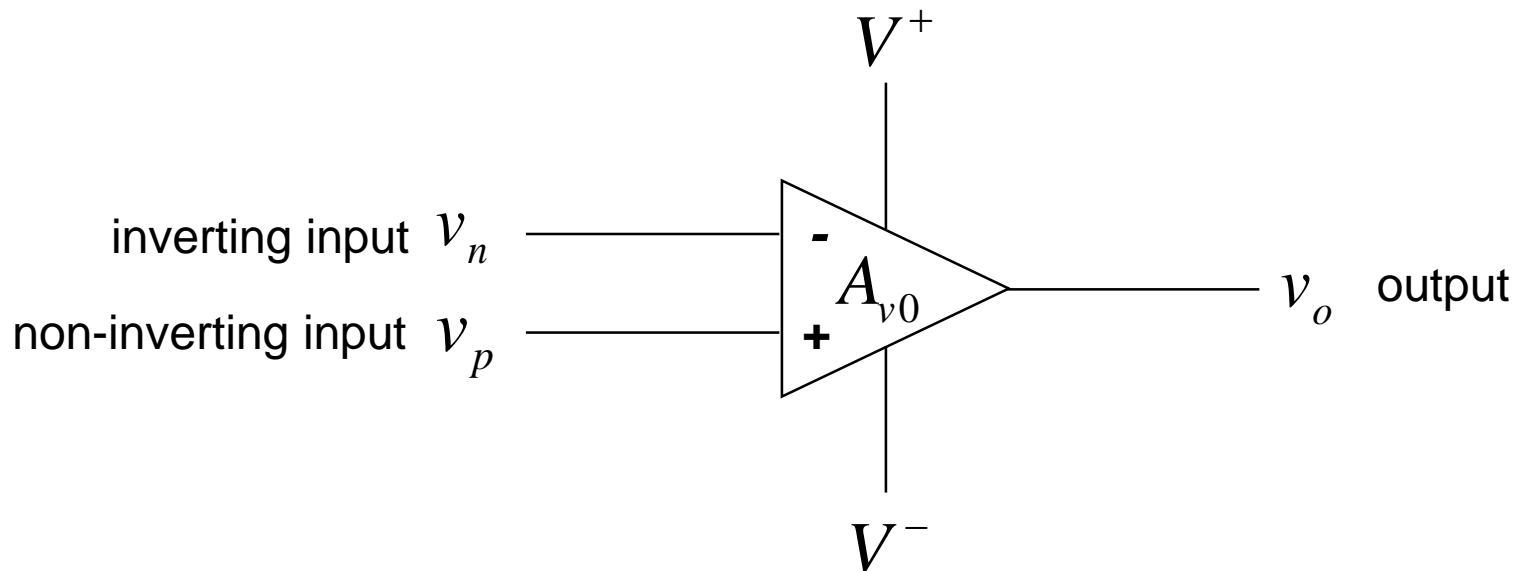

- differential input voltage:


$$v_d = v_p - v_n$$

- output voltage:

$$v_o = A_{v0} v_d = A_{v0} (v_p - v_n)$$

where A_{v0} = open loop voltage gain
(typically $10^5 - 10^8$ V/V at DC – ideally infinite)


Operational Amplifiers

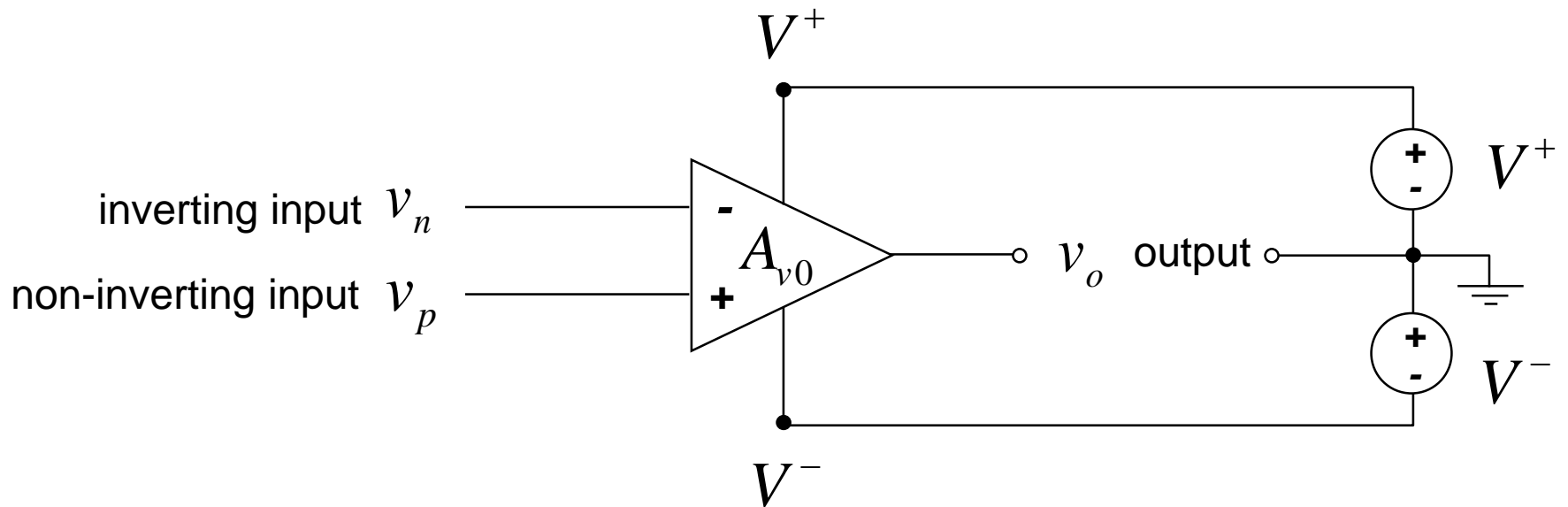



- Operational amplifiers are *active* devices.
- An op amp requires a DC power supply (V^+ and V^-), to bias internal transistors.

Operational Amplifiers

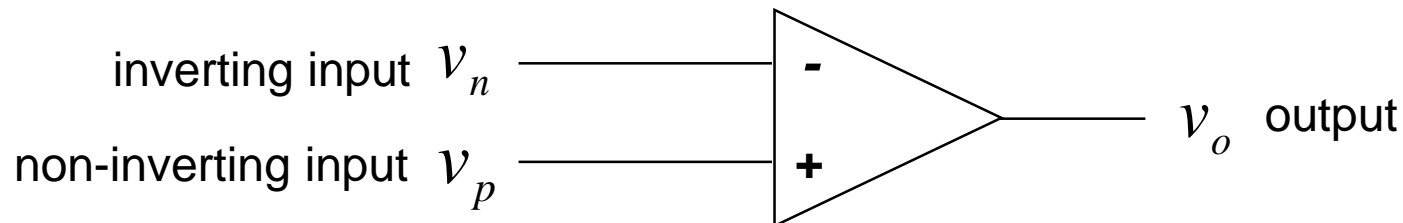- Power supply connections are often not explicitly shown in circuit diagrams, to reduce clutter. However, we must remember that the power supply terminals are always connected in a real circuit.




Operational Amplifiers

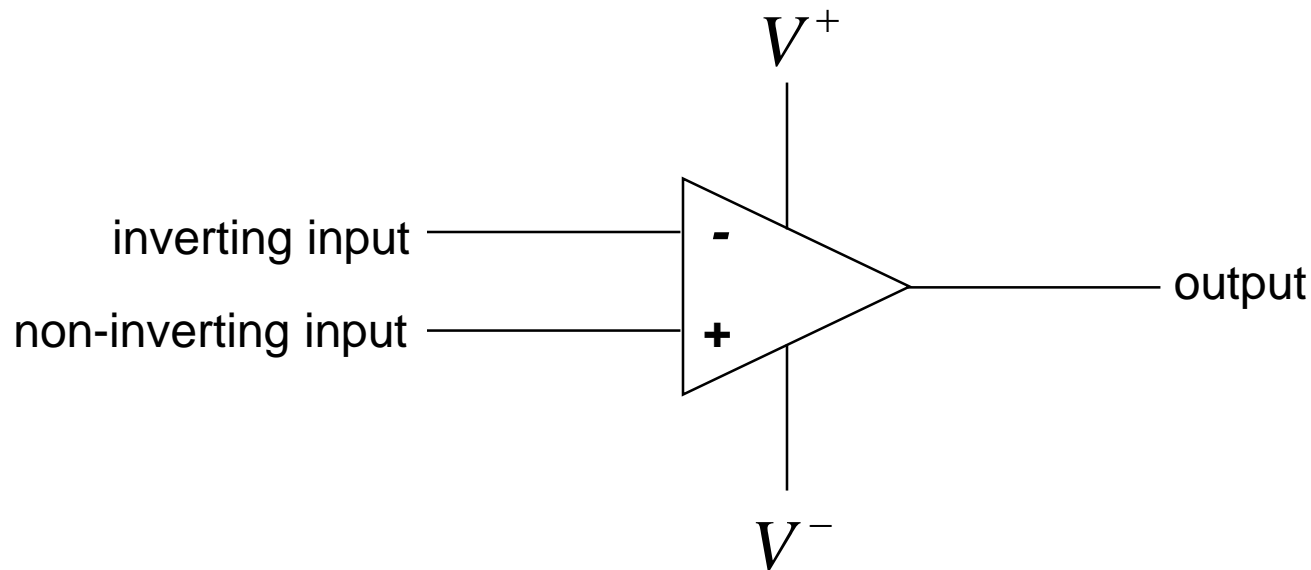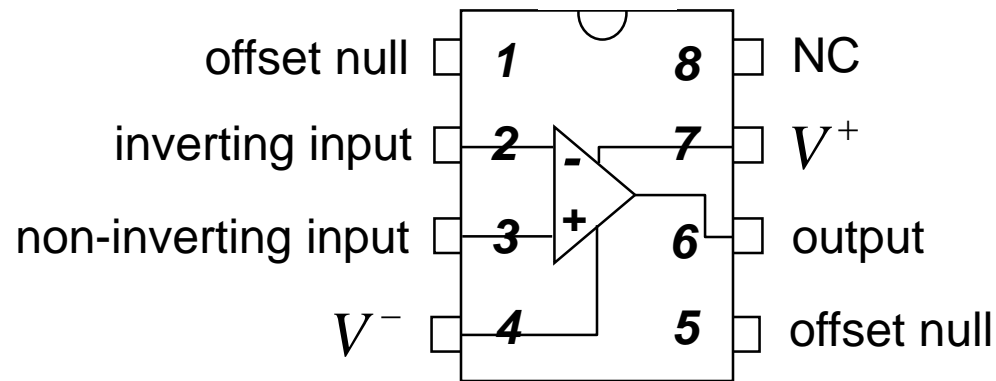

Operational Amplifiers


- Although we can think of an op amp as a single electronic device, internally it can consist of ~20-30 transistors (see μ A741 circuit on the next page)

Operational Amplifiers

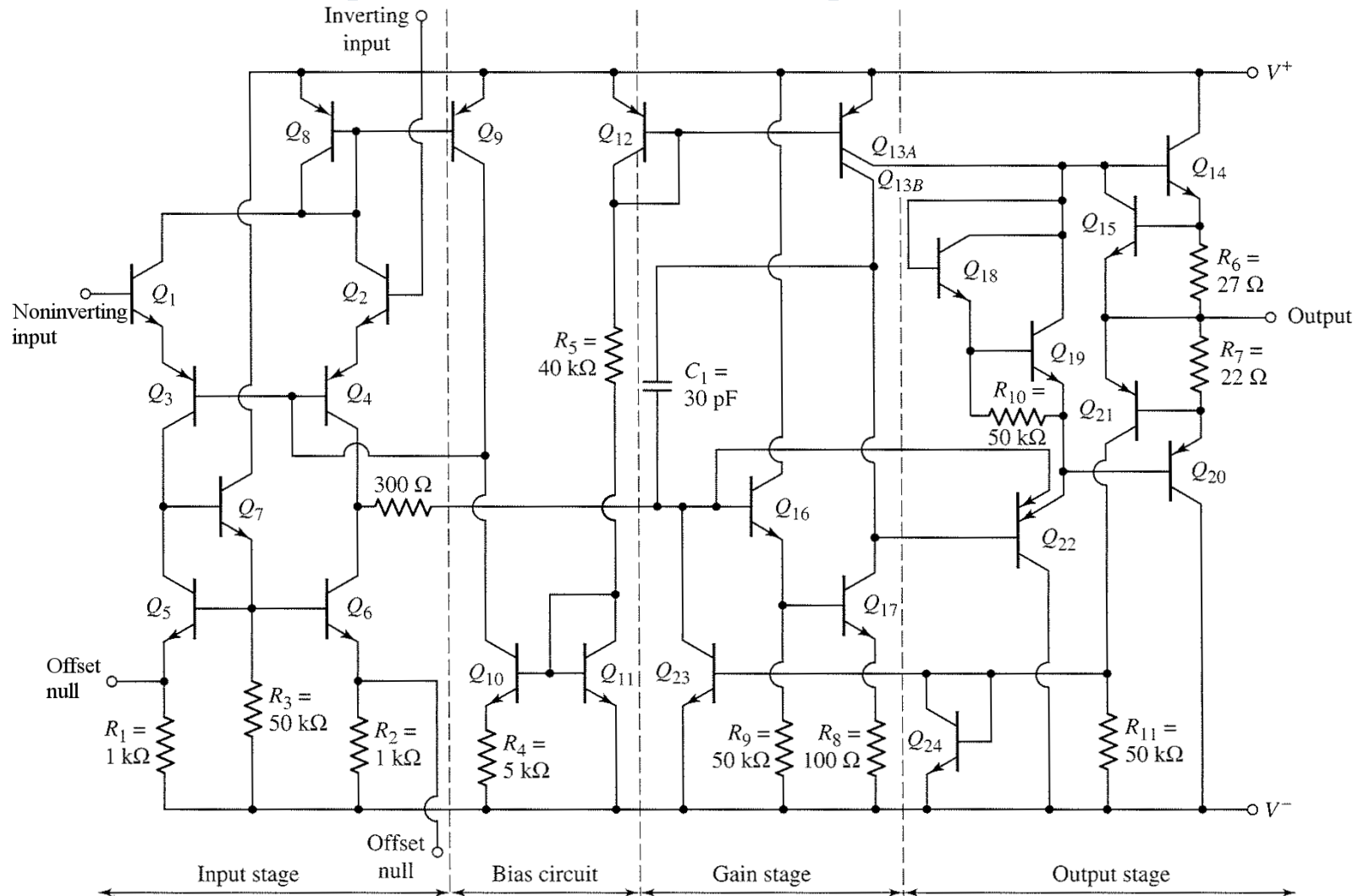

Schematic of the 741 Op Amp (Neamen, 3rd edition, p947).

Op Amp Equivalent Circuit

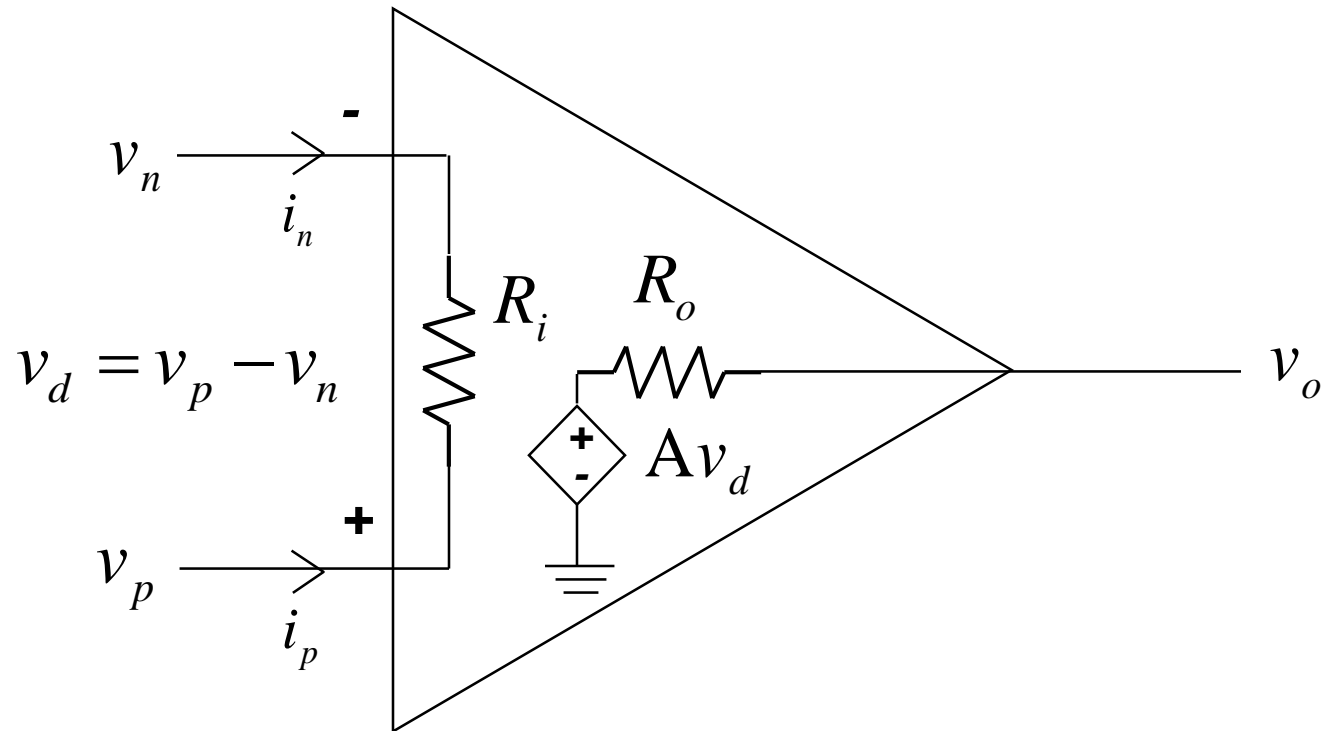


R_i = input resistance (typically $10^5 - 10^{13}\Omega$)

R_o = output resistance (typically $10 - 100\Omega$)

i_n and i_p are small (μA for BJT or pA for FET op amps)

Ideal Op Amp

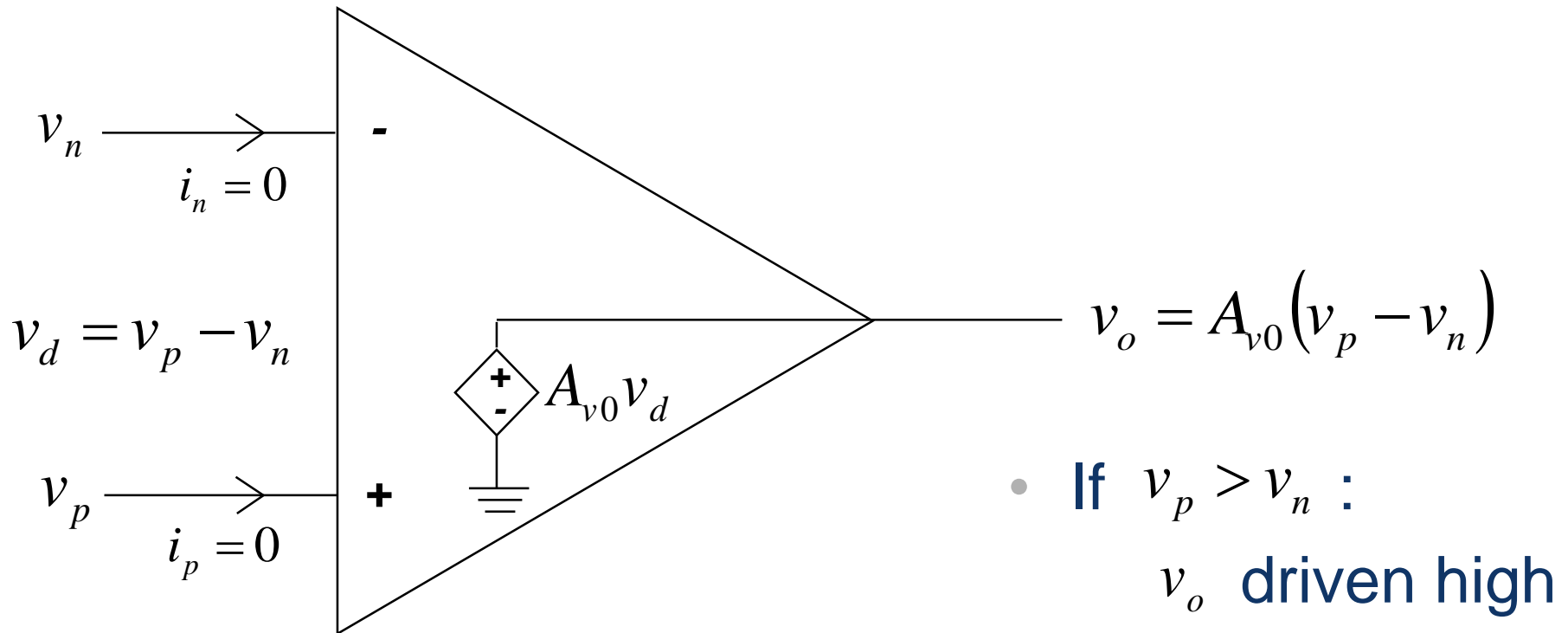


$$R_i = \infty, R_o = \infty$$

$$A = \infty$$


- **If** $v_n > v_p$:
 v_o driven low

Open Loop Behaviour

Non-ideal Op Amp, ie, A_{v0} is finite

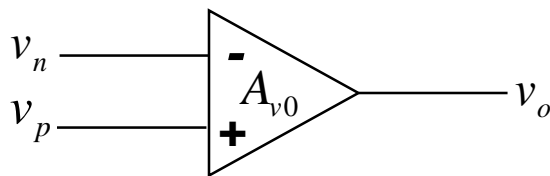

$$v_o = A_{v0}(v_p - v_n)$$

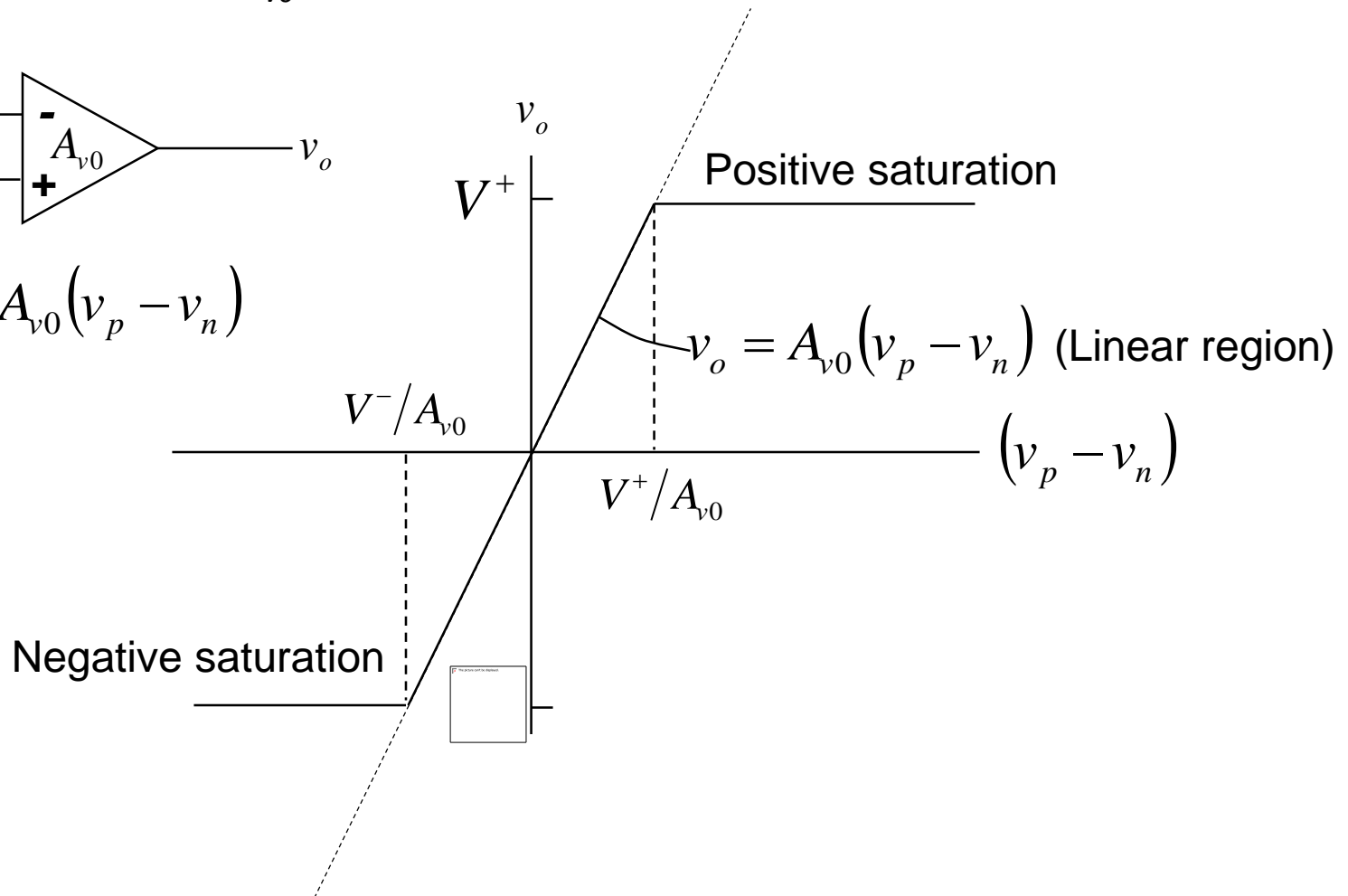


Closed Loop Mode


- In *closed loop* operation, a signal proportional to the output is connected back to one of the inputs.
- This is called *feedback*.

Negative Feedback

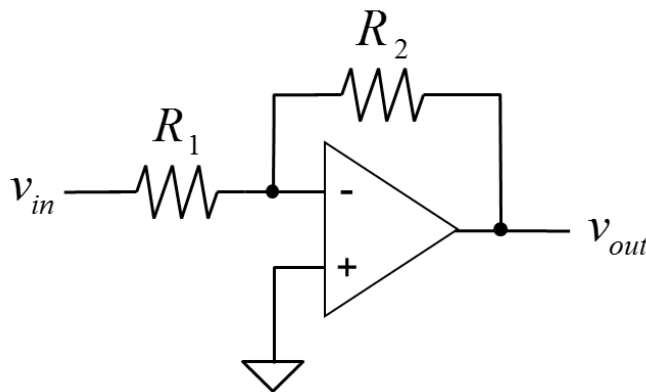- In Negative feedback, a signal proportional to the output is connected to the *inverting* input terminal.
-
- Negative feedback circuits:



inverting amplifier

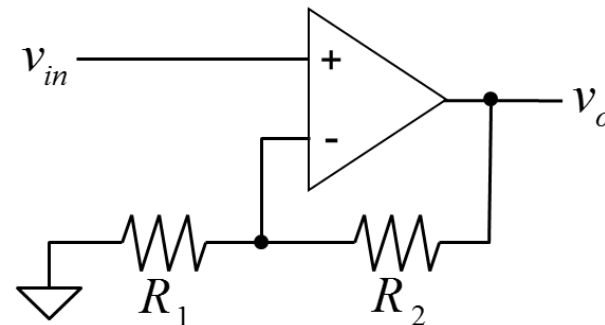

non-inverting amplifier

unity gain follower or buffer


Negative Feedback

- In Negative feedback, a signal proportional to the output is connected to the *inverting* input terminal.
- This forces the difference between the inputs $v_p - v_n$ to be almost zero.
- This effect where the op amp inputs are almost equal is called the ***virtual short condition***, i.e.:

$$v_n = v_p$$

Positive Feedback

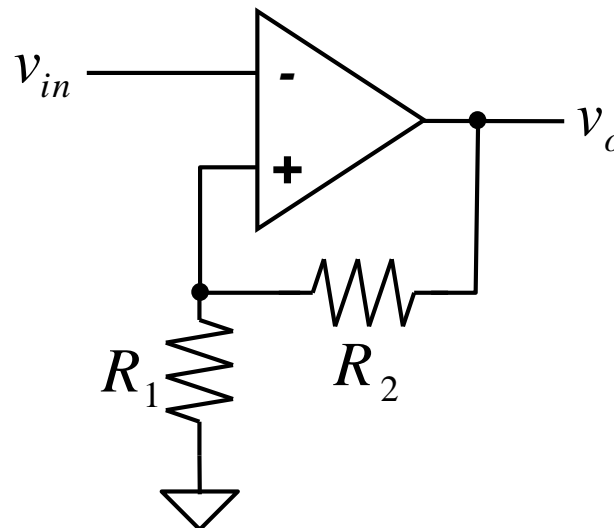- In Positive feedback, a signal proportional to the output is connected to the *non-inverting* input terminal.
- The effect is that the difference between the inputs becomes larger and the output reaches the positive saturation or the negative saturation value.
- Applications include the Schmitt trigger, square wave generator and pulse generator that will be discussed later.



Schmitt Trigger


Golden Rules

- “Golden Rules” of Op Amps with negative feedback:
 - I. The output attempts to do whatever is necessary to make the voltage difference between the inputs zero.
 - II. The inputs draw no current.

Cautions

- The “Golden Rules” do not apply if the op amp output is saturated at one of the supply rails.
- Need a feedback loop at DC or op amp will saturate.
- Some op amps have only a small maximum differential input voltage limit, $v_d = v_p - v_n$.
- Need bypass capacitors (eg, $1\mu\text{F}$) on the op amp supply rails, since inductances in the supply rails can lead to instabilities in the amplifiers.

Inverting Amplifier

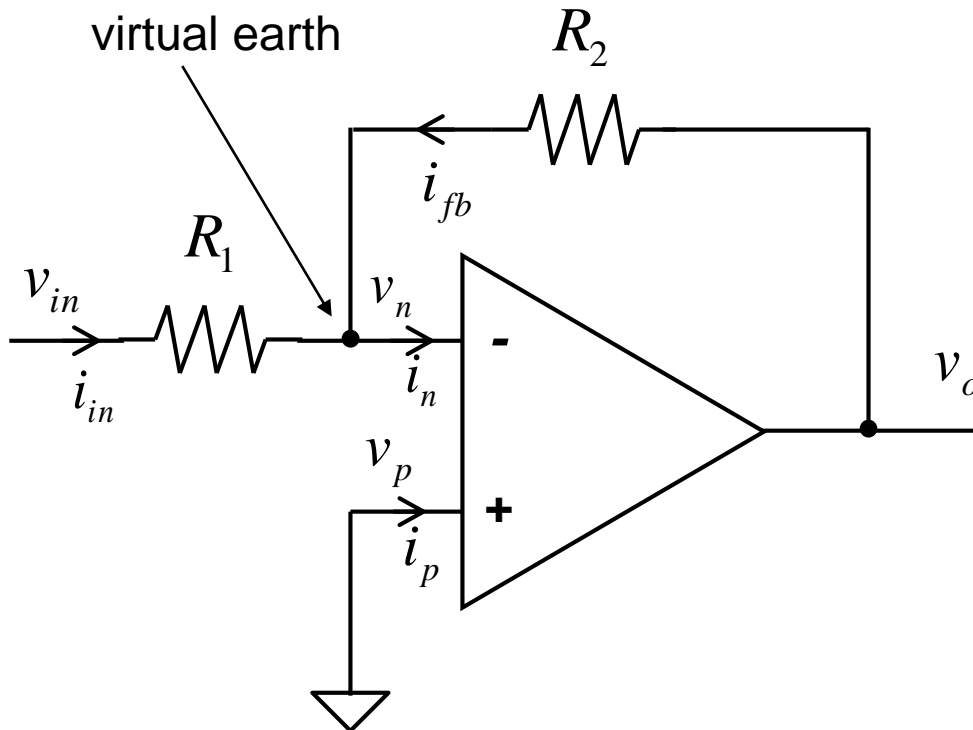

From Kirchhoff's Current Law,
and Golden Rule II:

From Golden Rule I: $v_n = 0$




Inverting Amplifier

- Negative feedback tends to make the inputs v_n and v_p equal.
- If v_p is incrementally greater than the v_n , output v_o will tend to be driven positive. If v_n is incrementally greater than the v_p , output v_o will tend to be driven negative.
- However the feedback through the R_2/R_1 voltage divider will cause v_o to be held at a value such that $v_n = v_p$.

Inverting Amplifier

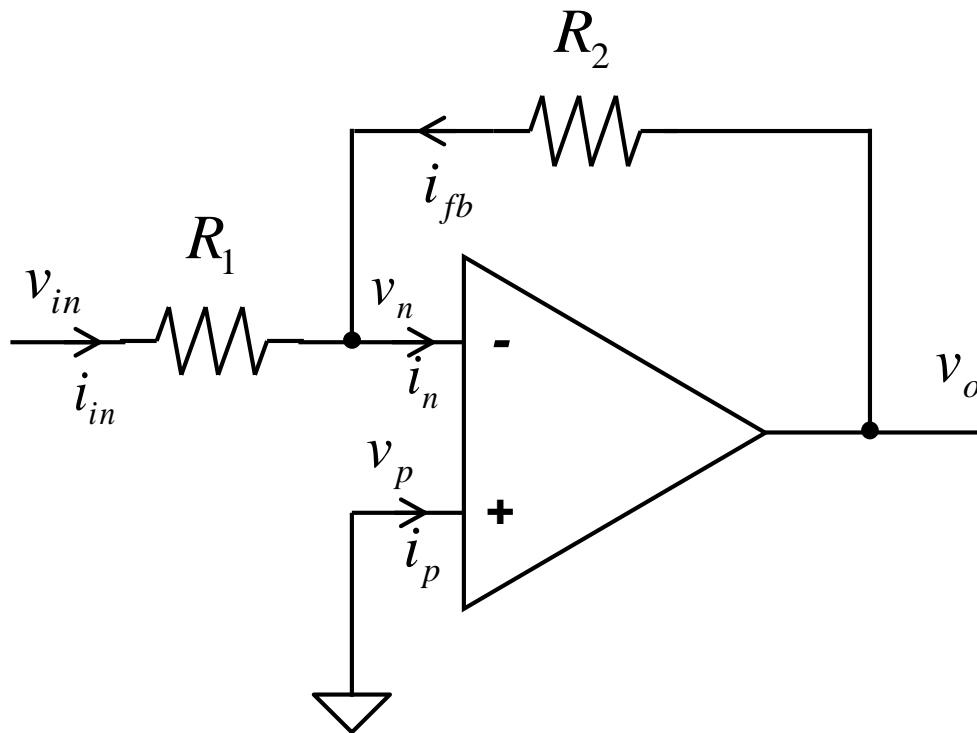- Example 1: Design an Op Amp circuit with a voltage gain of -10 .




Inverting Amplifier

- Values of resistors:
 - Theoretically, any resistor values that work out to give the gain we need would be OK.
 - Very small resistors (eg, 1Ω), are not practical because large currents would have to be supplied by the op amp. Currents of a few mA are usually acceptable.
 - Very large resistors (eg, $10\text{M}\Omega$), also present problems, their values can be unstable, input bias current can result in large offset voltages, and they are susceptible to pick up unwanted noise through stray capacitive coupling)
 - Generally, resistance values of 100Ω – $1\text{M}\Omega$ are suitable for most op amp circuits.

Non-inverting Amplifier

From the voltage divider rule:

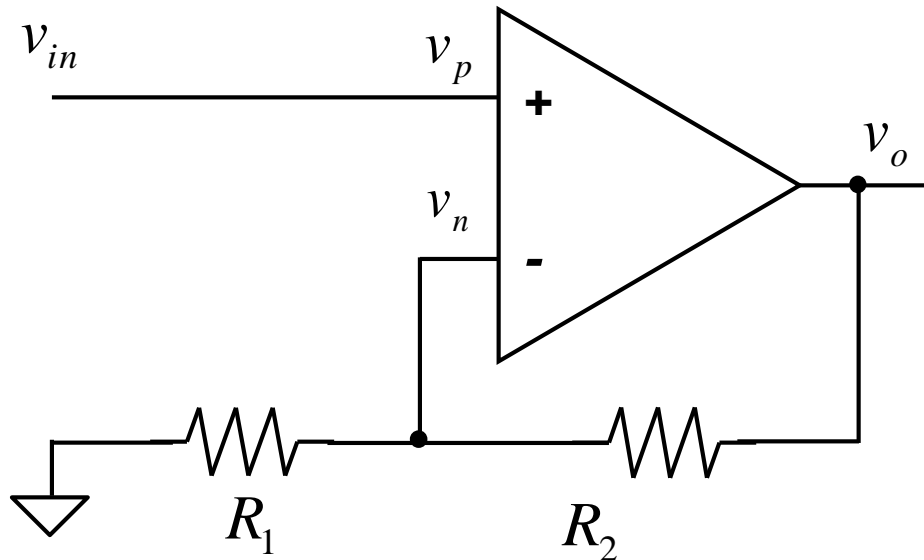


Since $v_{in} = v_p$, from Golden Rule I:




Non-inverting Amplifier

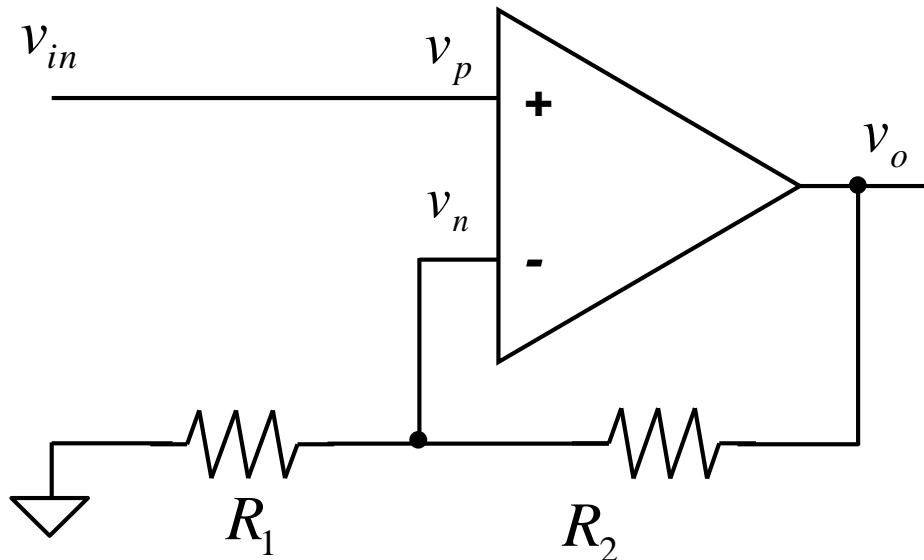Example 2: Design an Op Amp circuit with a voltage gain of 10.



Unity Gain Follower

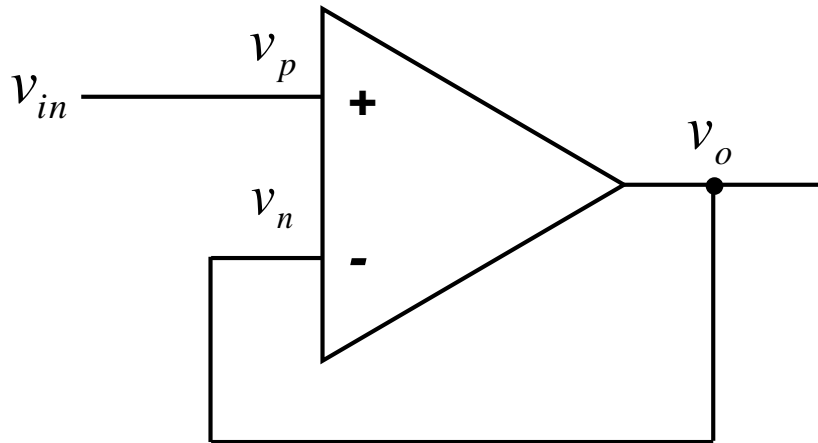



Since $v_{in} = v_p$ and $v_o = v_n$,
from Golden Rule I:

$$v_o = v_{in}$$



$$G_v = \frac{v_o}{v_{in}} = 1$$

- Used as a buffer because of its isolating properties (high input impedance, low output impedance)


Split Supply Op Amp

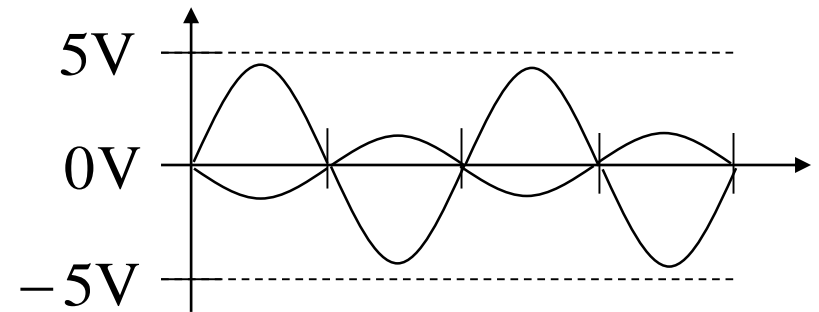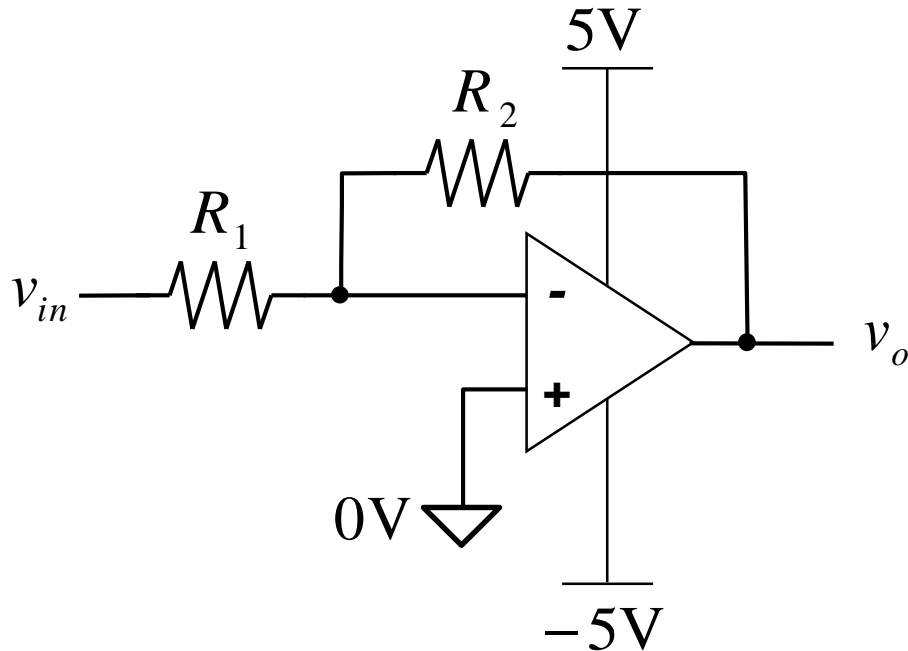


Single Supply Op Amp

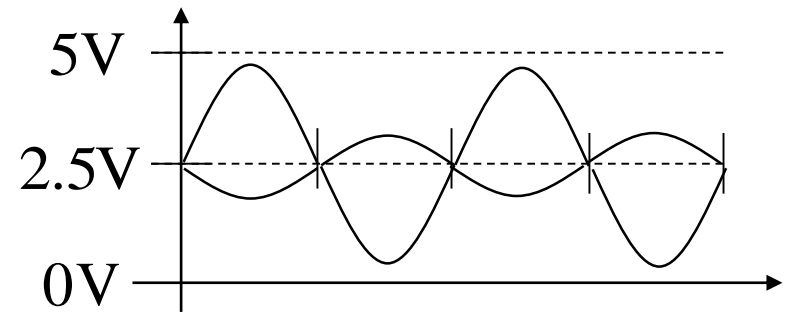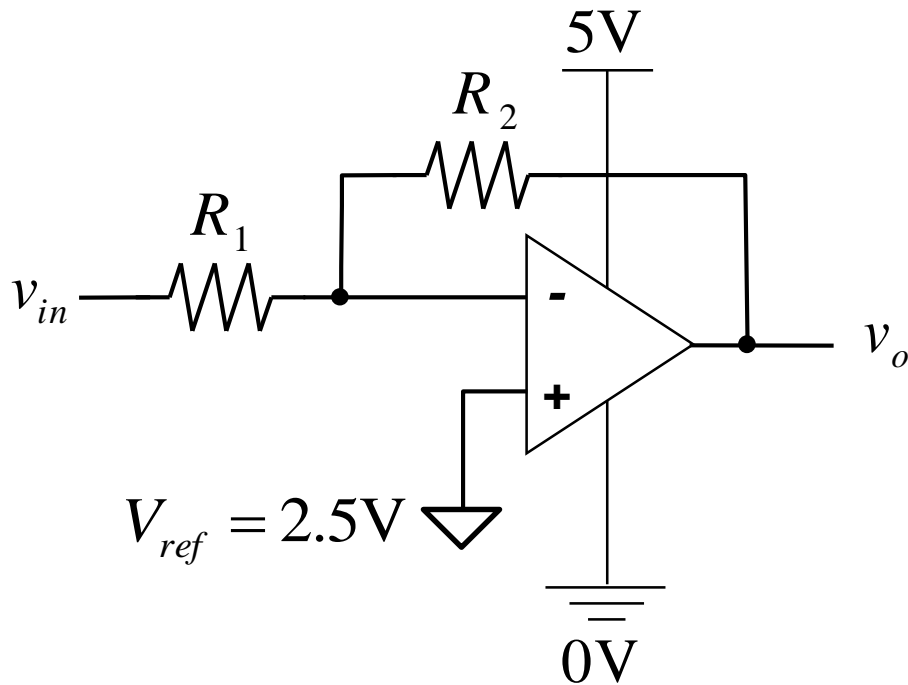

Op Amp Frequency Response – Open Loop

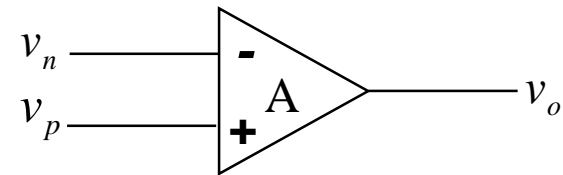

$$v_o = A(v_p - v_n)$$

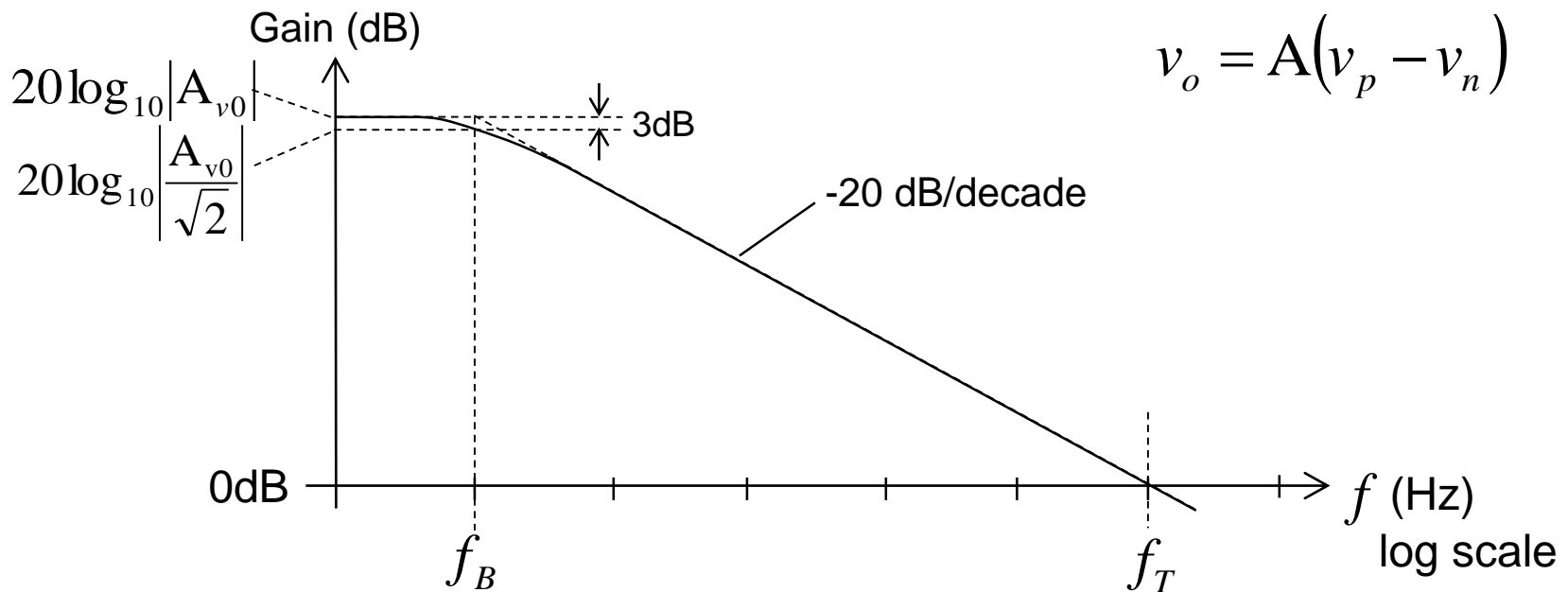


Op Amp Frequency Response – Open Loop

- Non ideal op amp:
 - f_T = gain BW product
 - At frequency = f_T , the gain is 1
 - Typical values: $f_T = 1\text{MHz}$, $A = 10^5$, $f_B = 10\text{Hz}$


Op Amp Frequency Response – Closed Loop Amplifier

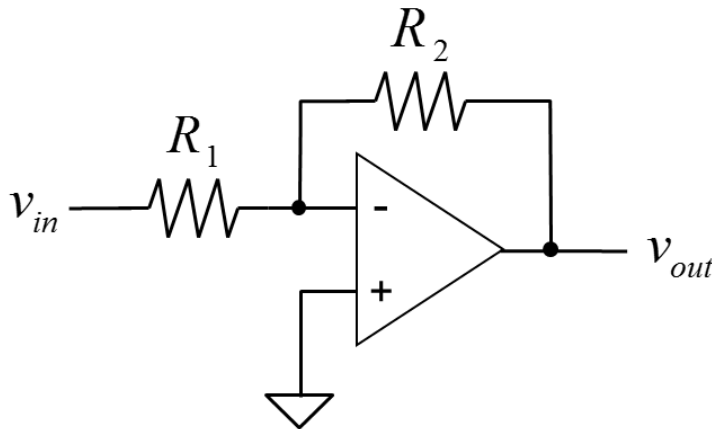- Non-ideal op amp, inverting and non-inverting amplifiers:



inverting amplifier

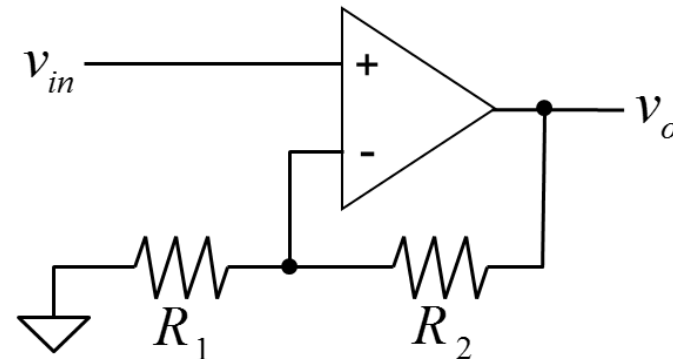
closed loop gain:
$$G = \frac{v_o}{v_{in}} = -\frac{R_2}{R_1}$$




non-inverting amplifier

closed loop gain:
$$G = \frac{v_o}{v_{in}} = 1 + \frac{R_2}{R_1}$$

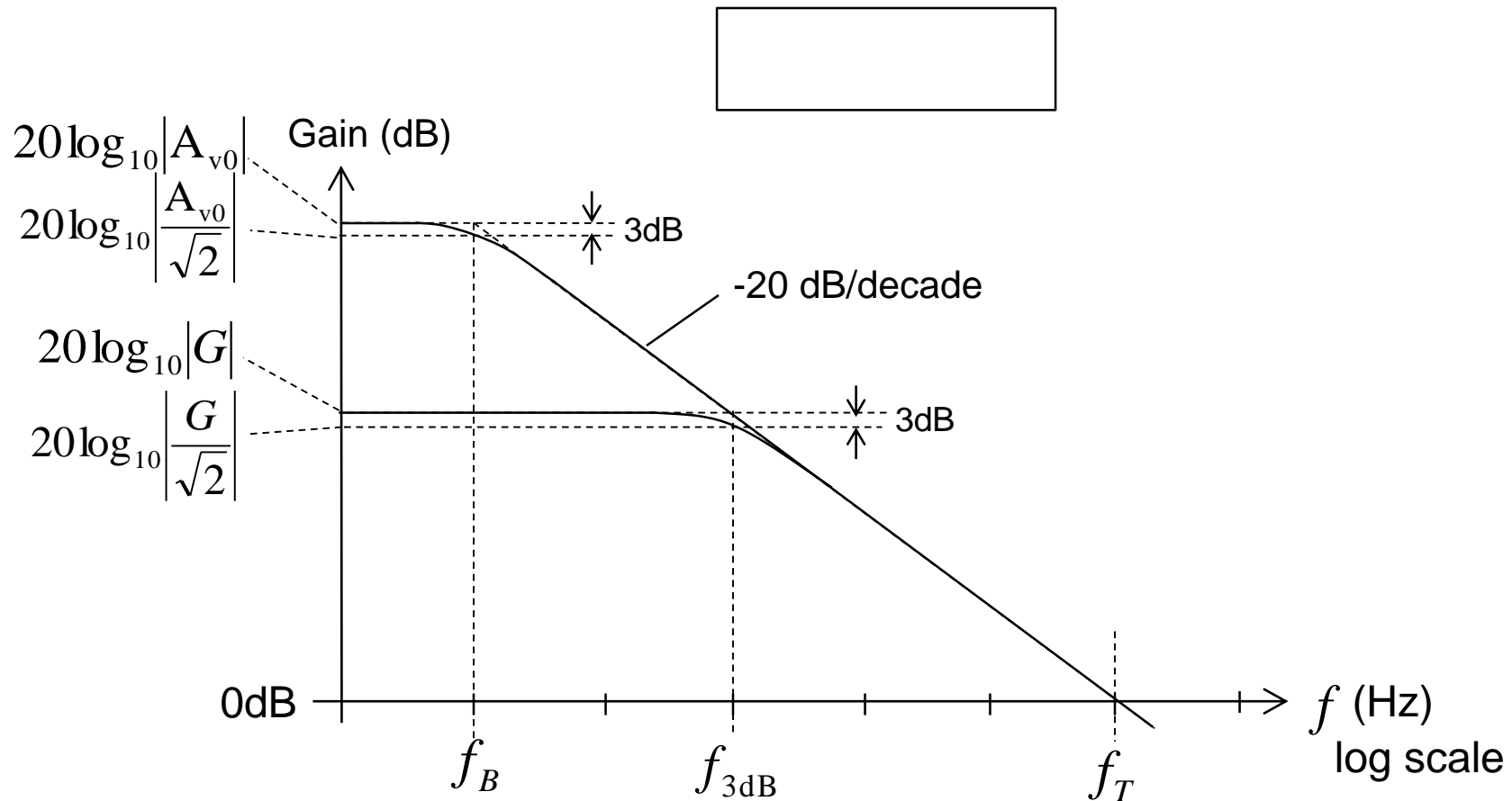Op Amp Frequency Response – Closed Loop Amplifier




Op Amp Frequency Response – Closed Loop

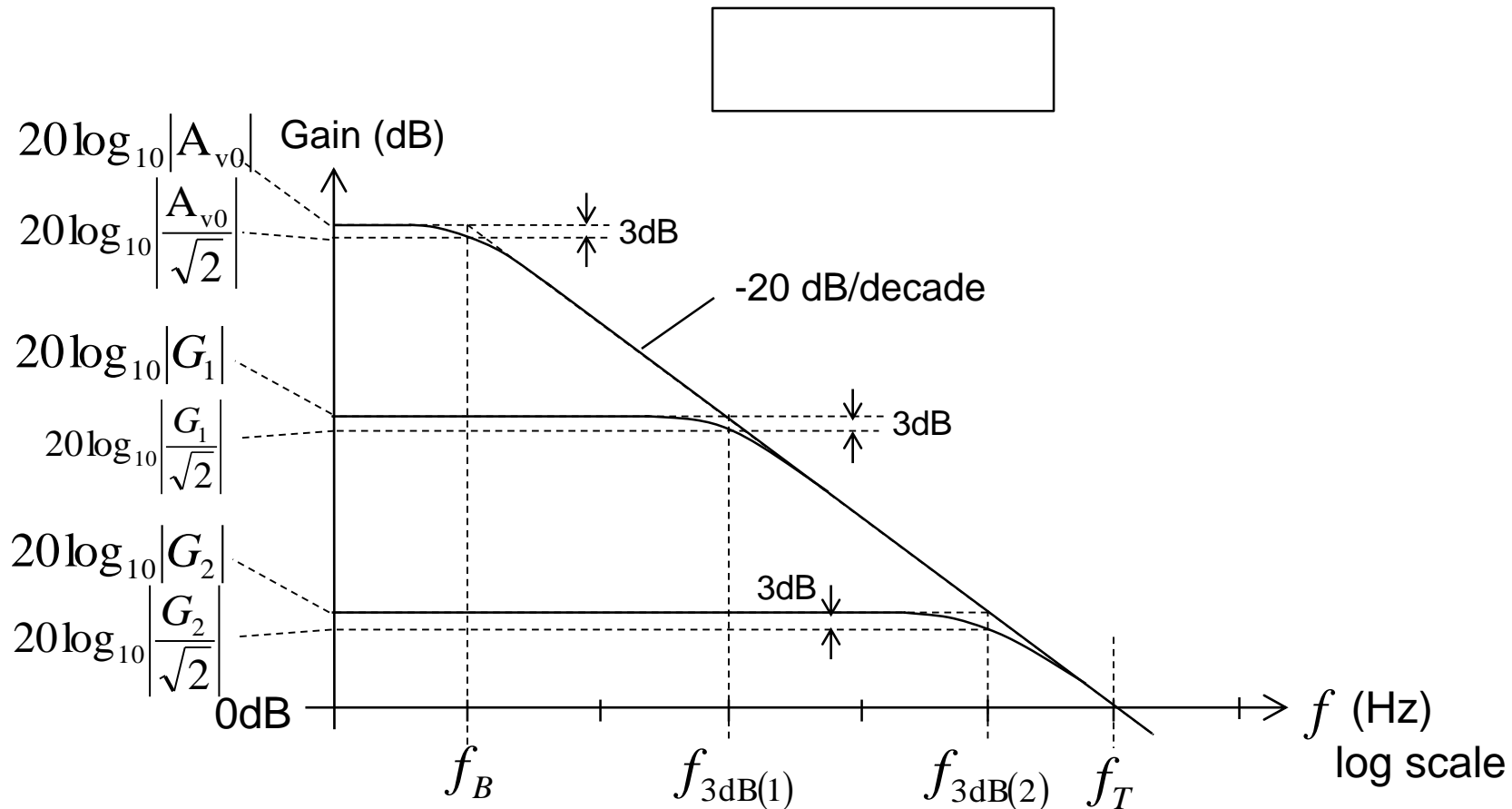

Op Amp Frequency Response – Closed Loop

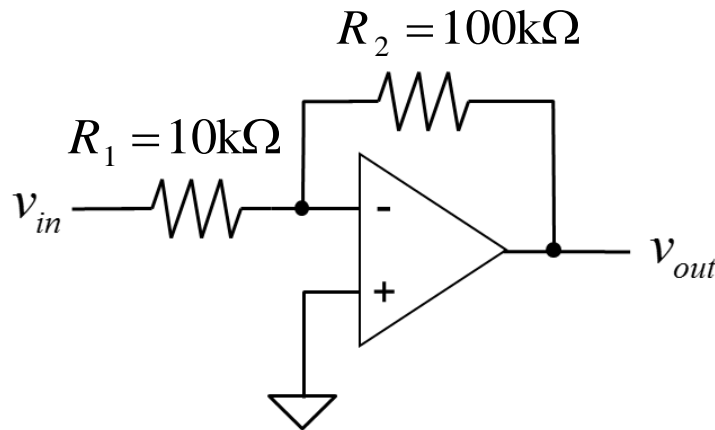- Example 3: An op amp has a gain bandwidth product $f_T = 1\text{MHz}$, $A_{v0} = 10^5$ and $f_B = 10\text{Hz}$. This op amp is used in an inverting amplifier, with $R_1 = 10\text{k}\Omega$ and $R_2 = 100\text{k}\Omega$. What is the 3dB bandwidth of the inverting amplifier?



inverting amplifier

closed loop gain:

$$G = \frac{v_o}{v_{in}} = -\frac{R_2}{R_1} = -\frac{100\text{k}}{10\text{k}} = -10$$

Op Amp Frequency Response – Closed Loop

- Example 3:

