



**School of Electrical Engineering and
Robotics**


EGB348 Electronics

**Additional Filter Circuits
Jasmine Banks**

Recommended Readings:

Summing Biquads

- Consider the summing circuit:

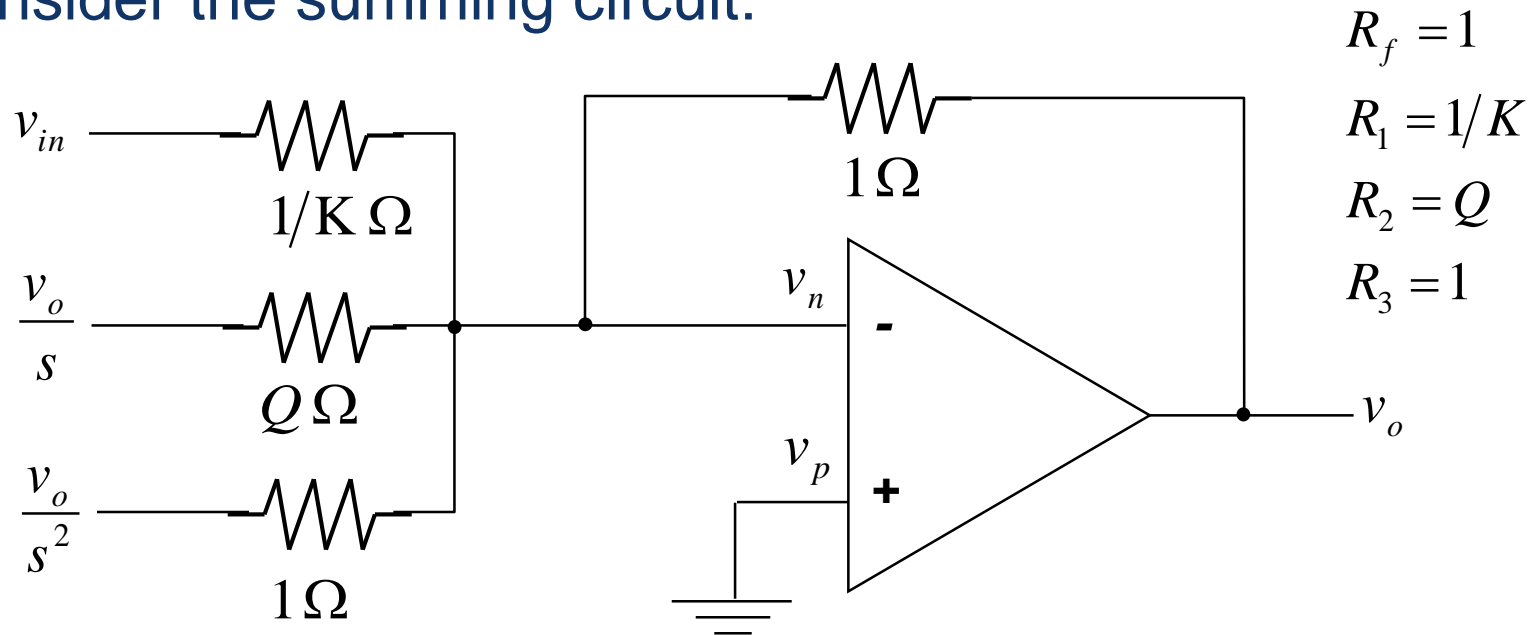

$$v_o = - \left(\frac{R_f}{R_1} v_{in1} + \frac{R_f}{R_2} v_{in2} + \frac{R_f}{R_3} v_{in3} \right) = - \left(K v_{in} + \frac{v_o}{Qs} + \frac{v_o}{s^2} \right)$$

Summing Biquads


- Rearranging:

$$v_o \left(1 + \frac{1}{Qs} + \frac{1}{s^2} \right) = -K v_{in}$$

$$\frac{v_o}{v_{in}} = \frac{-K}{1 + \frac{1}{Qs} + \frac{1}{s^2}} = \frac{-Ks^2}{s^2 + \frac{s}{Q} + 1}$$

- This is a high pass filter

Summing Biquads

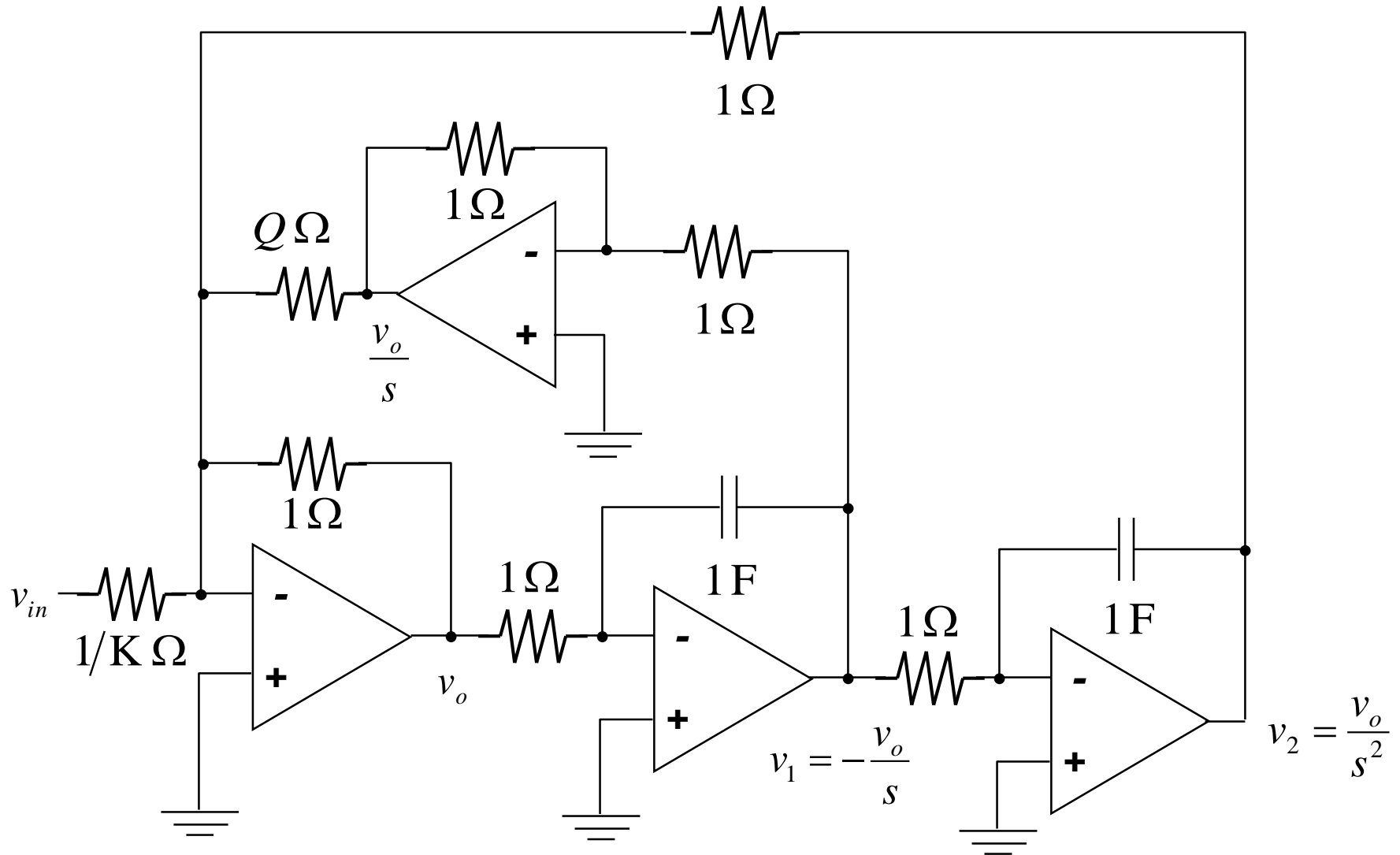

Summing Biquads

- Output v_1 :

$$v_1 = -\frac{v_o}{s} = \left(-\frac{1}{s} \right) \frac{-Ks^2}{\left(s^2 + \frac{s}{Q} + 1 \right)} v_{in}$$

$$\frac{v_1}{v_{in}} = \frac{-Ks}{s^2 + \frac{s}{Q} + 1}$$

- This is a band pass output.

Summing Biquads

- Output v_2 :

$$v_2 = -\frac{v_o}{s^2} = \left(\frac{1}{s^2} \right) \frac{-Ks^2}{\left(s^2 + \frac{s}{Q} + 1 \right)} v_{in}$$


$$\frac{v_2}{v_{in}} = \frac{-K}{s^2 + \frac{s}{Q} + 1}$$

- This is a low pass output.

Summing Biquads

- If we only need band pass and low pass outputs, we can use the following circuit.
- This is called the Tow-Tomas biquad.

Summing Biquads

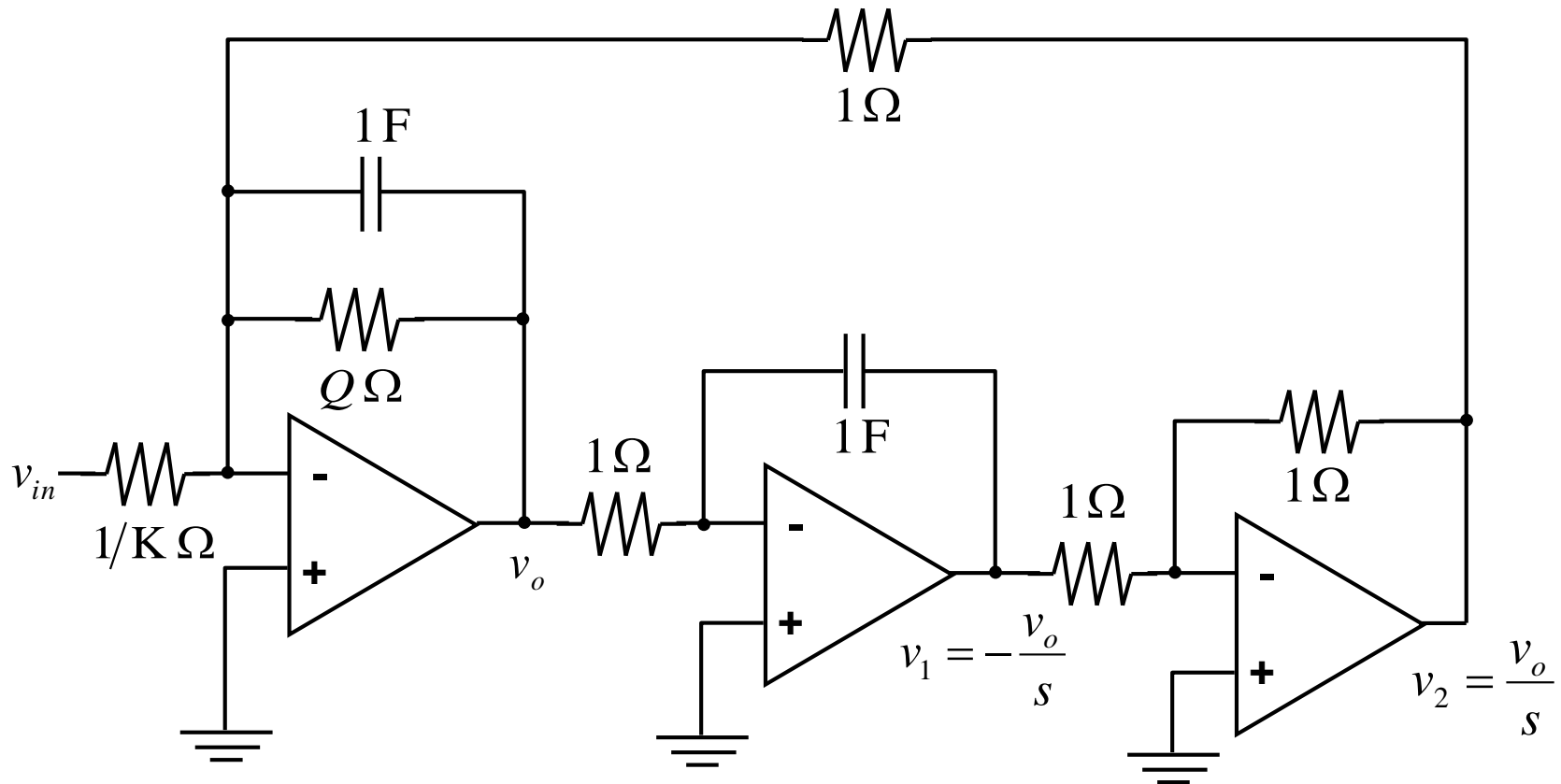

Summing Biquads

- From:

$$v_o = -\left(\frac{Z_f}{Z_1} v_{in1} + \frac{Z_f}{Z_2} v_{in2}\right)$$

- Where:

$$Z_f = \frac{Q}{1 + sQ}$$

$$v_{in1} = v_{in}$$

$$Z_1 = 1/K$$

$$v_{in2} = \frac{v_o}{s}$$

$$Z_2 = 1$$

Summing Biquads


- we have:
$$v_o = \frac{-Q}{1+sQ} \left(Kv_{in} + \frac{v_o}{s} \right)$$
- re-arranging:
$$\frac{v_o}{v_{in}} = \frac{-Ks}{s^2 + s/Q + 1}$$
- Also, since $v_2 = \frac{v_o}{s}$:
$$\frac{v_2}{v_{in}} = \frac{-K}{s^2 + s/Q + 1}$$

Multiple Feedback (MFB) Filters

- Alternative to VCVS (Sallen Key)
- Less sensitive to component variations
- Have one component fewer in the design
- Produce an additional 180° phase shift.

Multiple Feedback (MFB) Filters


- General circuit:

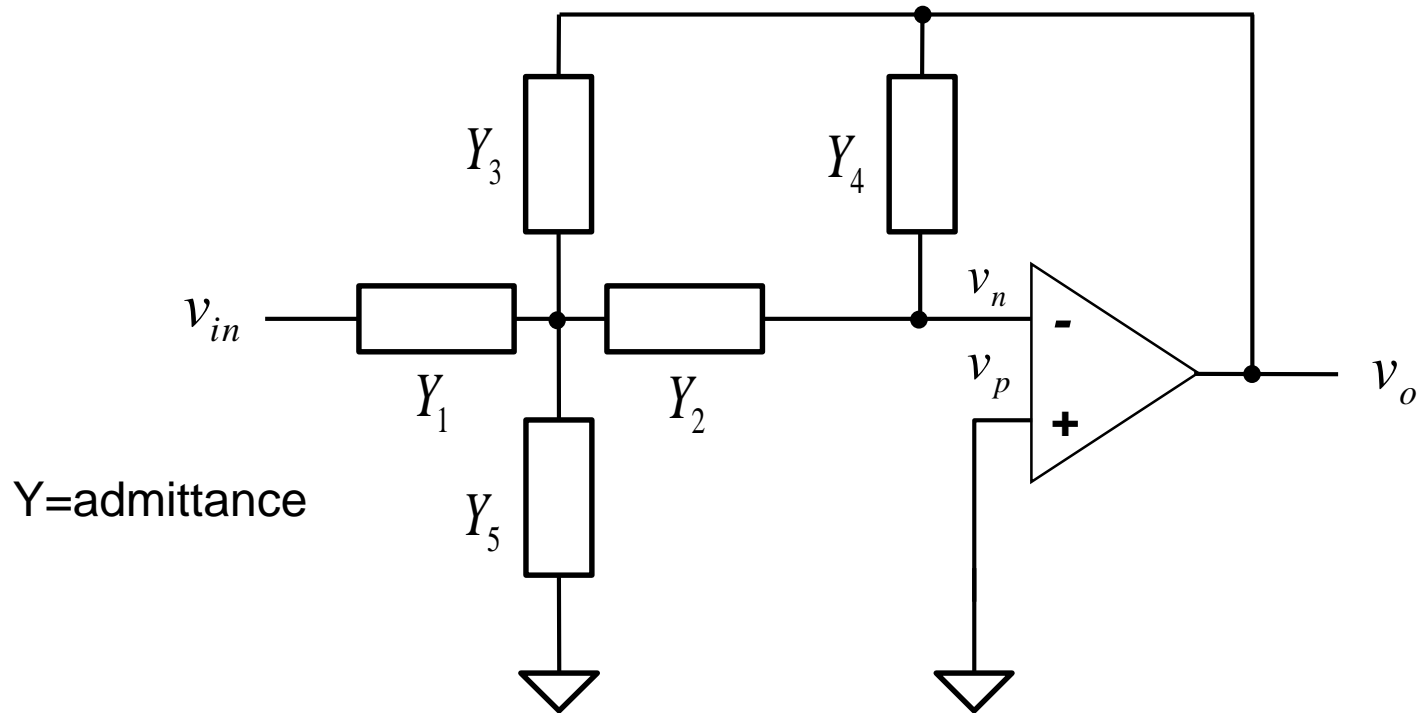

$$\frac{v_o}{v_{in}} = \frac{Y_1 Y_2}{Y_4 (Y_1 + Y_2 + Y_3 + Y_5) + Y_2 Y_3}$$

Multiple Feedback (MFB) Filters


- Low pass:

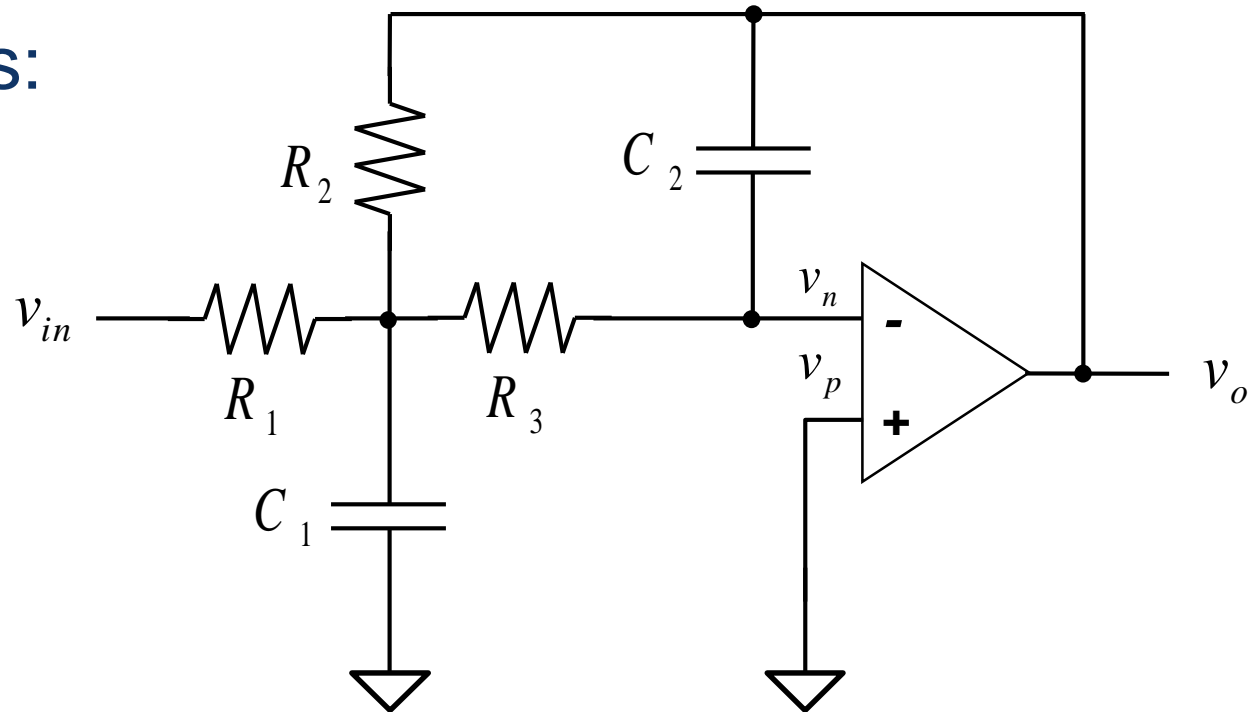

$$\frac{v_o}{v_{in}} = \frac{-\frac{1}{C_1 C_2 R_1 R_3}}{s^2 + s \left(\frac{1}{C_1 R_1} + \frac{1}{C_1 R_2} + \frac{1}{C_1 R_2} \right) + \frac{1}{C_1 C_2 R_2 R_3}}$$

Multiple Feedback (MFB) Filters


- High pass:

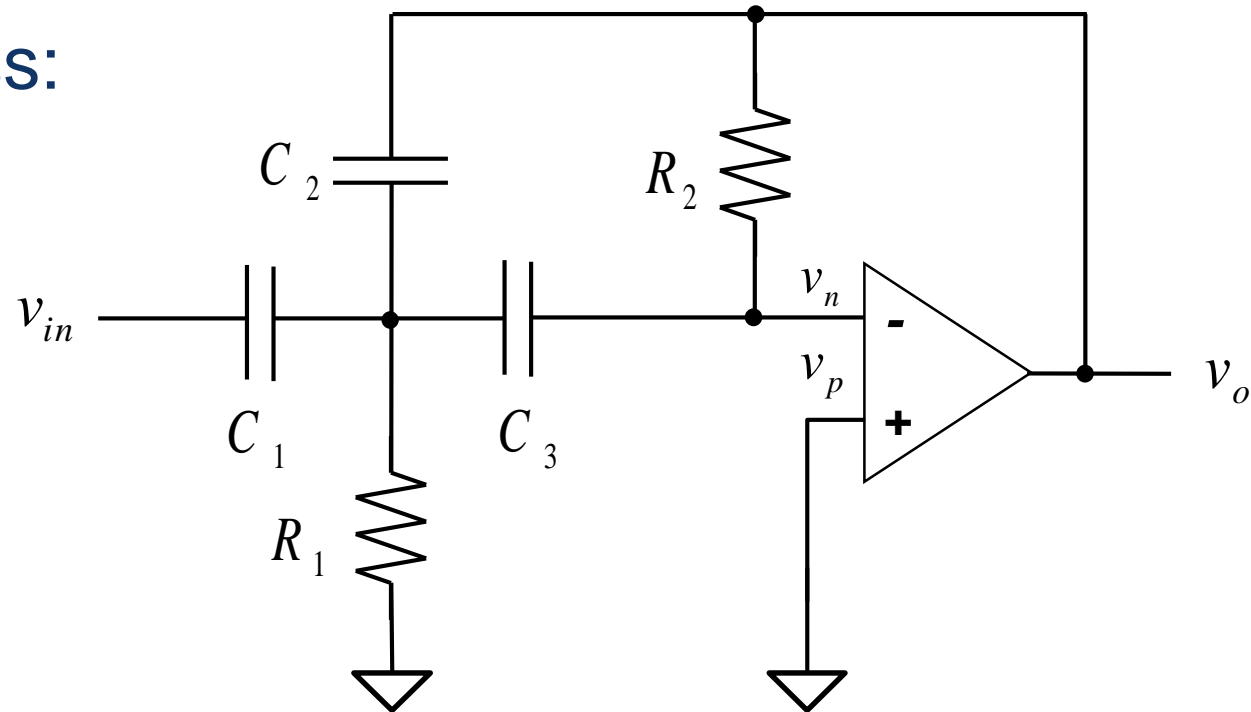

$$\frac{v_o}{v_{in}} = \frac{-s^2 \frac{C_1}{C_2}}{s^2 + s \frac{(C_1 + C_2 + C_3)}{C_2 C_3 R_2} + \frac{1}{R_1 R_2 C_2 C_3}}$$

Multiple Feedback (MFB) Filters

- Band pass:

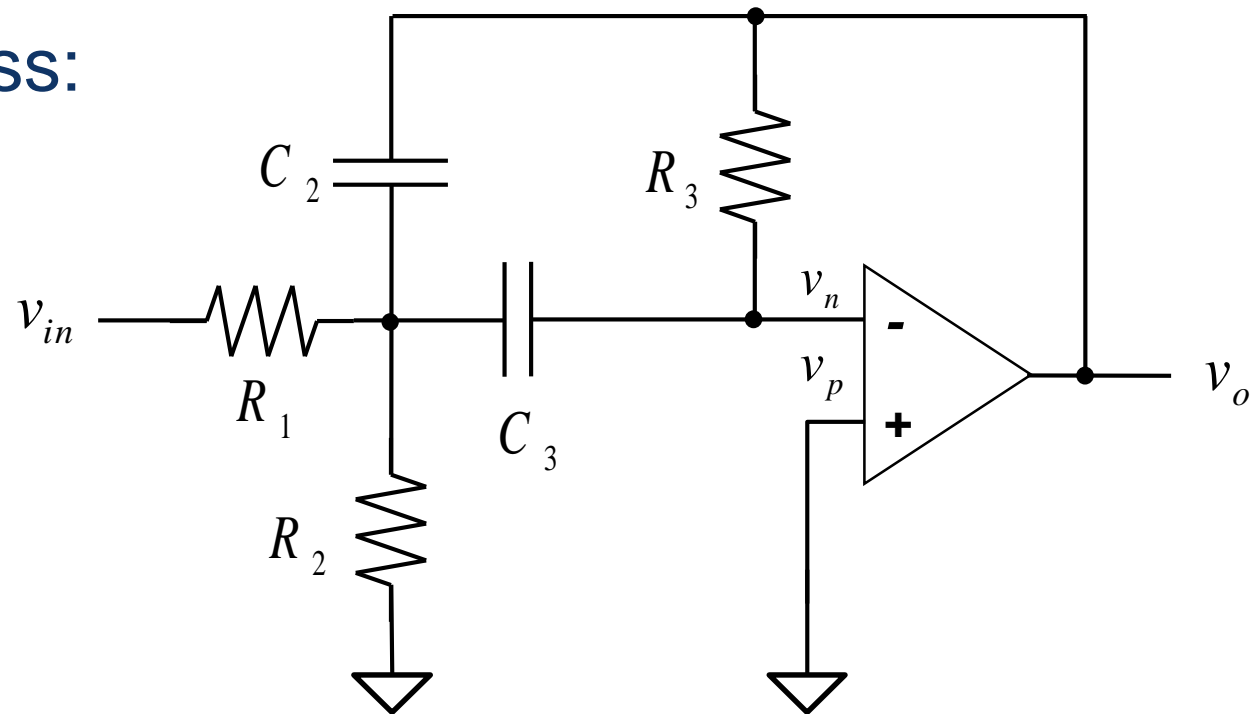

$$\frac{v_o}{v_{in}} = \frac{-s \frac{1}{C_1 R_1}}{s^2 + s \frac{(C_1 + C_2)}{C_1 C_2 R_3} + \frac{(R_1 + R_2)}{C_1 C_2 R_1 R_2 R_3}}$$